
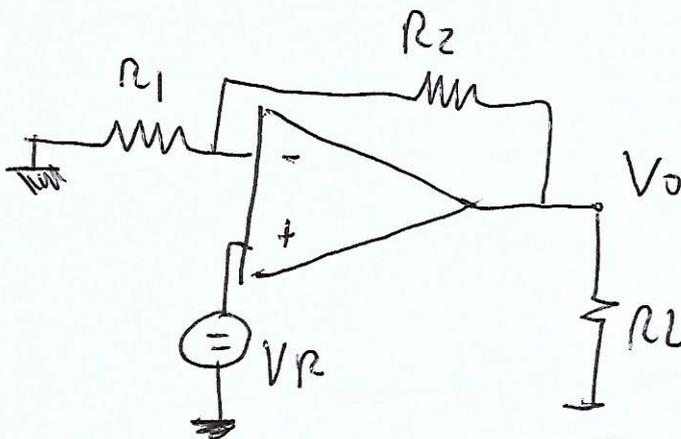


# Fuente regulada serie

## Con Amplificador Operacional

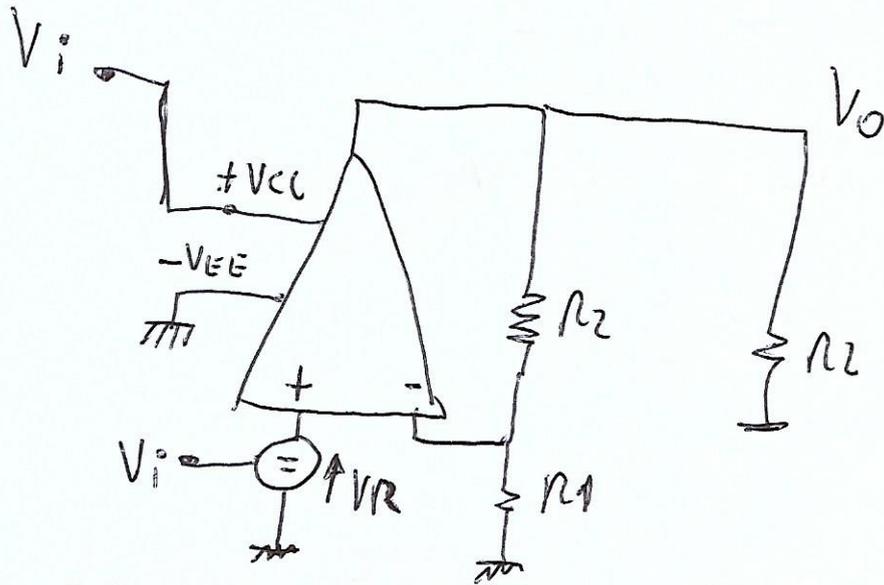

$$V_o = V_R \left( 1 + \frac{R_2}{R_1} \right)$$


$$V_i \begin{cases} +50\% \\ -15\% \end{cases}$$

$$V_{D0} = V_i - V_o$$

Para regular se considera  $V_{i \min}$

= calcular disipador se considera  $V_{i \max}$

# Resistencia de Salida

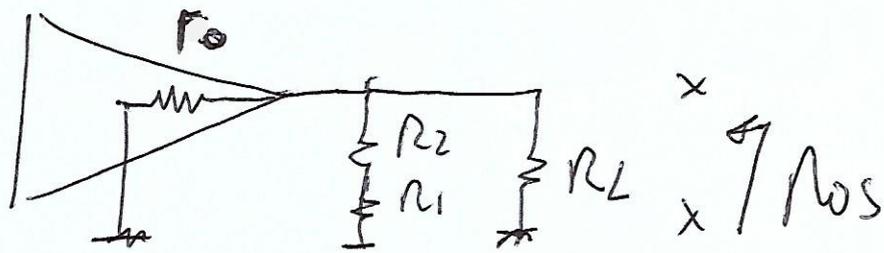


$$R_{os} = R_L // (R_1 + R_2) // r_o$$

$$R_{osf} = R_{os} / D$$

Si:  $R_o = 75 \Omega$  y  $D = 10^4$


$$R_{os} < 75 \Omega \therefore R_{osf} \leq 7.5 \text{ m}\Omega$$

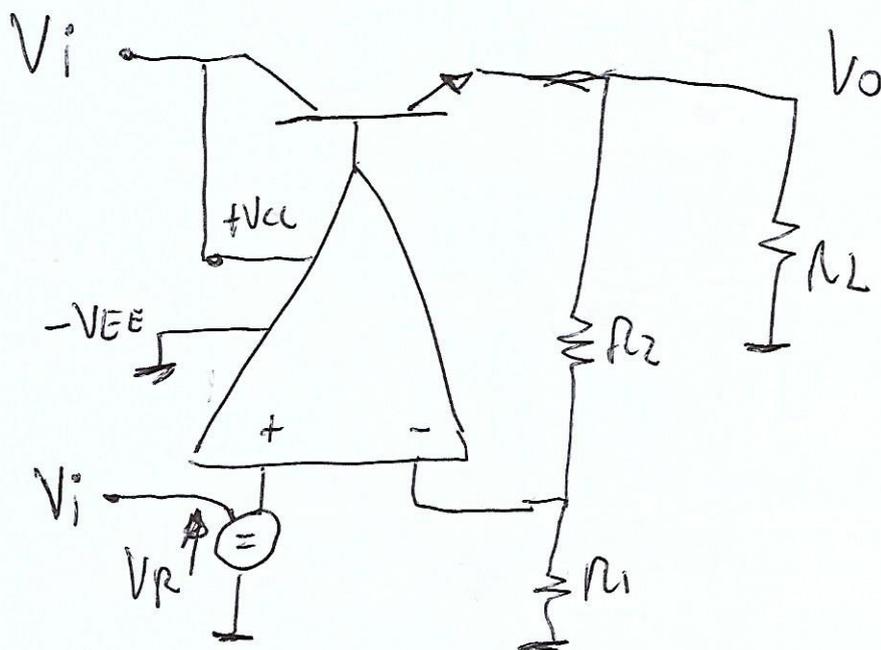Con Amplificador Operacional y Transistor de paso



$$V_o = V_r \left( 1 + \frac{R_2}{R_1} \right)$$

Resistência de saída

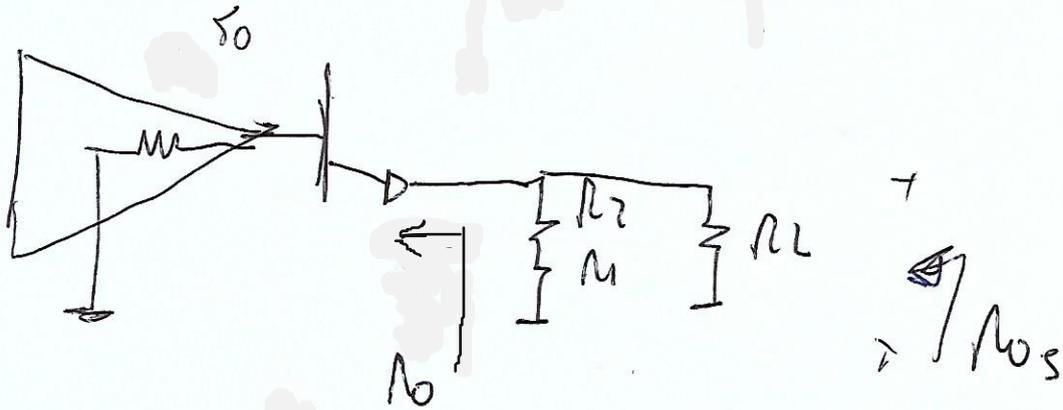


$$R_o = h_{ib} + \frac{r_o}{1+h_{fe}}$$

Para SA  $h_{ib} = 25\text{m}\Omega$  s.  $r_o = 75\Omega$   
 s.  $h_{fe} = 100$   $r_o < 1\Omega$

$$R_{os} = R_o // (R_2 + R_1) // R_L \approx R_o \quad R_{osf} = R_{os} / \beta$$


$$A_D = 10^4 \quad R_{osf} < 100\mu\Omega$$

Con limitador de corriente

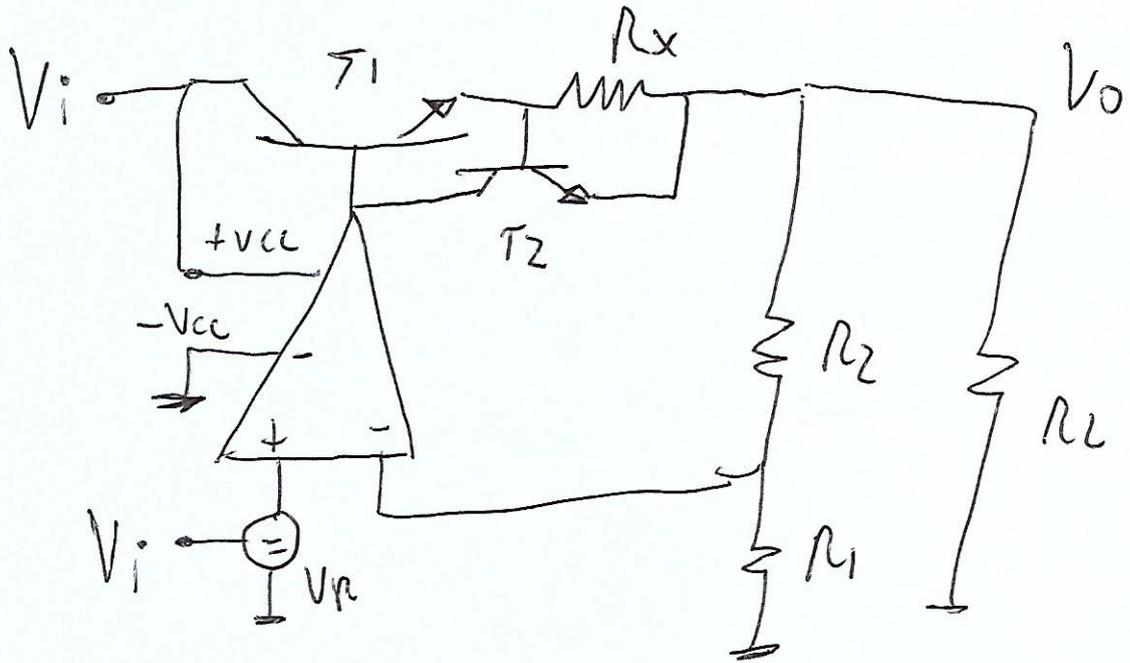

$$V_o = V_r \left( 1 + \frac{R_2}{R_1} \right)$$

R salida

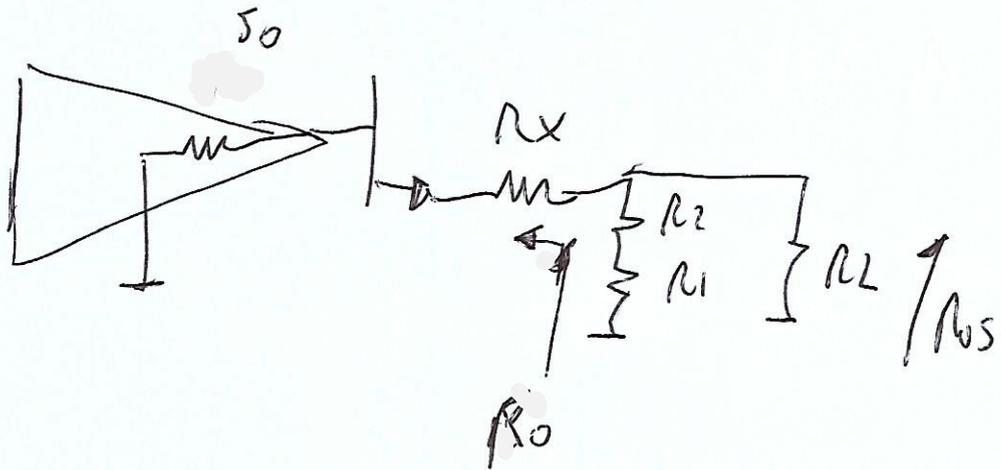


$$R_o = R_x + h_{ib} + \frac{r_o}{1+h_{fe}} \quad \text{with } R_x = 0,47 \Omega$$


$$R_o < 1,5 \Omega \quad R_s < 1,5 \Omega \quad \text{with } \beta = 10^4$$

$$R_{osf} < 150 \mu\Omega$$

# Regulador de tres terminales

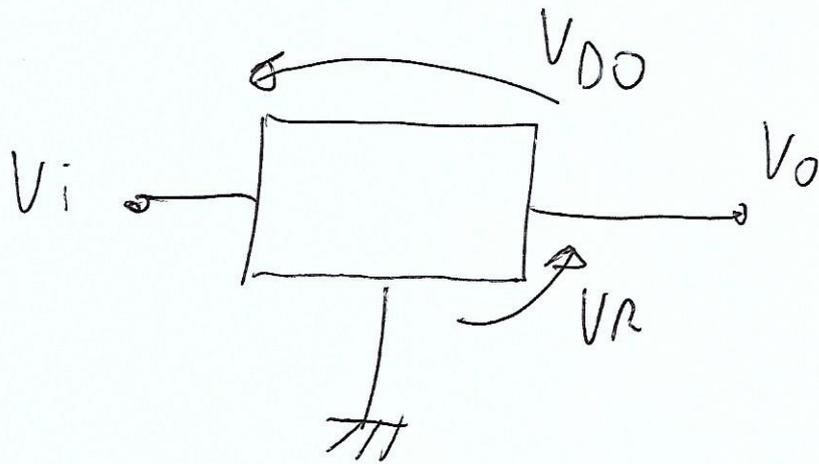

Para obtener otro valor de \$V\_o\$

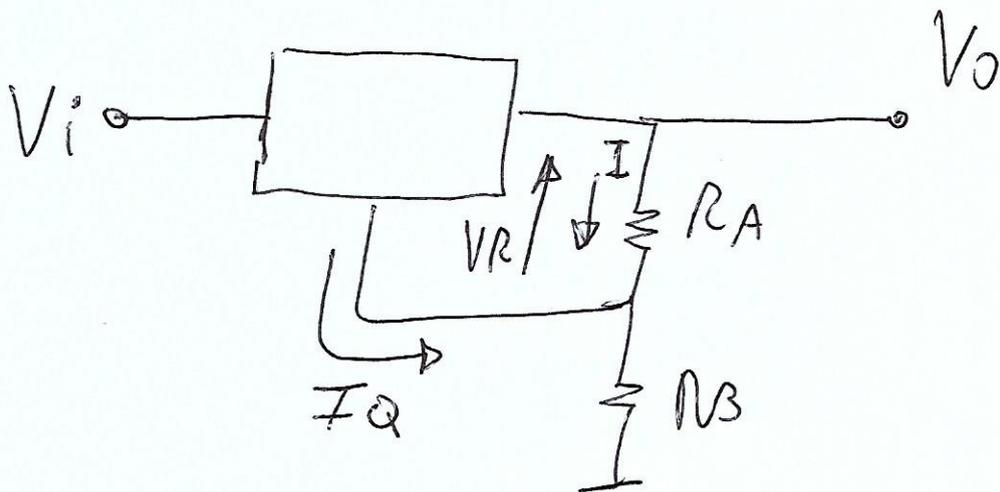

$$\wedge I \gg I_Q \quad I = \frac{V_R}{R_A}$$

$$V_o = I (R_A + R_B)$$

$$V_o = \frac{V_R}{R_A} (R_A + R_B) \quad V_o = V_R \left( 1 + \frac{R_B}{R_A} \right)$$

\$I\_Q\$ en fijos    \$I\$ adj en variables